

EE719: Mixed-Signal VLSI Design

Course Project

Manideep Vudayagiri, 190070074

February 10, 2022


Design of unit cell Analog circuitry for the 8-bit segmented DAC

PART 1

(Made changes in values from the previous submission)

Last digit of roll no. = 4 $\Rightarrow R_L = 25 + 4 = 29 \Omega$, $C_L = 1 + \frac{4}{10} = 1.4 pF$

Calculating V_{FS} , I_{LSB}

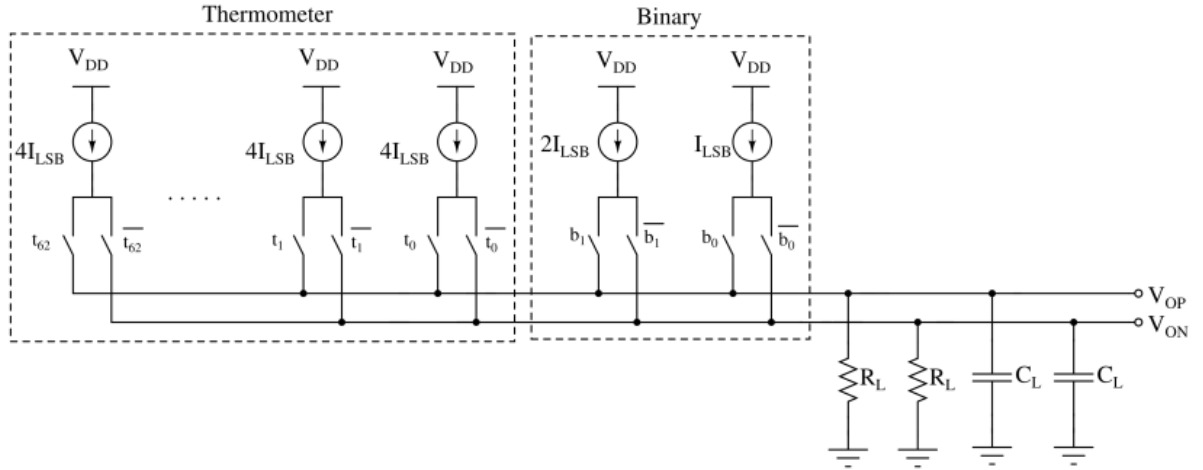

From the 8-bit DAC circuit diagram,

$$V_{out} = V_{OP} - V_{ON}$$

$$(V_{out})_{max} = 0 - 255I_{LSB}R_L = -255I_{LSB}R_L, \quad (\text{Digital input} = 0)$$

$$(V_{out})_{min} = 255I_{LSB}R_L - 0 = +255I_{LSB}R_L, \quad (\text{Digital input} = 255)$$


$$\Rightarrow \text{Output voltage swing} = V_{FS} = (V_{out})_{max} - (V_{out})_{min} = 510I_{LSB}R_L$$

$$\text{Given, } V_{FS} > 0.8 V_{pp} \Rightarrow I_{LSB} > \frac{0.8}{510 \times 29}$$

$$\Rightarrow I_{LSB} > 54.1 \mu A$$

 ----- (1)

Now, we can find an upper limit on I_{LSB} as follows



Switch circuit in the DAC unit cell

From the above circuit, in saturation,

$$V_{ON} \mid V_{OP} = V_{DD} - ((V_{dsat})_{M_{B1}} + (V_{dsat})_{M_{B2}} + (V_{dsat})_{M_1} \mid (V_{dsat})_{M_2})$$

Minimum possible voltage at V_{ON} or V_{OP} is $\frac{0.8V}{2} = 0.4V$ ($V_{DD} = 1.2V$)

$$\Rightarrow 1.2V - \Sigma V_{dsat} > 0.4V$$

$$\Rightarrow \Sigma V_{dsat} < 0.8V$$

The overdrive voltage (or V_{dsat}) for the cascode transistors M_{B1} and M_{B2} has to be between 200-300 mV and the same for the switching transistors has to be 50-100 mV

(ref. Razavi's paper)

We can choose $(V_{dsat})_{M_{B1}} = (V_{dsat})_{M_{B2}} = 200mV$ and $(V_{dsat})_{M_1} = (V_{dsat})_{M_2} = 90mV$ to satisfy the above conditions.

$$\Rightarrow \Sigma V_{dsat} = 200mV + 200mV + 90mV = 490mV$$

That makes $(V_{ON})_{max} = (V_{OP})_{max} = 1.2 - 0.490 = 0.710V$

$$\Rightarrow 255I_{LSB}R_L < 0.710$$

$$\Rightarrow I_{LSB} < \mu A$$

------(2)

From (1) and (2)

$$\Rightarrow 54.1\mu A < I_{LSB} < \mu A$$

I choose

$$\boxed{I_{LSB} = 57 \mu A}$$

$$\Rightarrow V_{FS} = 510 I_{LSB} R_L$$

$$\boxed{V_{FS} = 0.843 V}$$

Calculating W/L

$$(I_D)_{sat} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} V_{dsat}^2 \quad (\mu_p C_{ox} = 140 \frac{\mu A}{V^2})$$

For M_{B1}, M_{B2}

$$\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (0.2)^2 = 57 * 10^{-6} \Rightarrow \frac{W_1}{L_1} = 20.36$$

-----(3)

For M_1, M_2

$$\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (0.09)^2 = 57 * 10^{-6} \Rightarrow \frac{W_2}{L_2} = 100.53$$

-----(4)

Expression for INL_{max}

From Pelgrom's paper,

$$\frac{\sigma_{I_D}^2}{I_D^2} = \frac{4\sigma_{V_{TH}}^2}{(V_{GS} - V_{TH})^2} + \frac{\sigma_{\beta}^2}{\beta^2}, \quad \frac{\sigma_{\beta}^2}{\beta^2} \approx \frac{A_{\beta}^2}{WL} + S_{\beta}^2 D^2$$

Neglecting S_{β} ,

$$\Rightarrow \frac{\sigma_{I_D}^2}{I_D^2} = \frac{4\sigma_{V_{TH}}^2}{(V_{GS} - V_{TH})^2} + \frac{A_{\beta}^2}{WL} = \frac{4\sigma_{V_{TH}}^2}{(V_{GS} - V_{TH})^2} + \frac{A_{\beta}^2}{WL}$$

From Razavi's paper,

$$INL_{max} = \frac{\sigma_{I_u}}{2I_u} \sqrt{2^N} LSB \quad (N = 8)$$

$$\Rightarrow INL_{max} = 8 \sqrt{\frac{4A_{V_{TH}}^2}{WL(V_{GS} - V_{TH})^2} + \frac{A_{\beta}^2}{WL}} LSB$$

$$(A_{\beta} = 4\% \mu m, \quad A_{V_{TH}} = 4.6 mV - \mu m)$$

Required: $INL_{max} < 1 LSB$

$$\Rightarrow 8 \sqrt{\frac{4A_{V_{TH}}^2}{W_1 L_1 (V_{GS} - V_{TH})^2} + \frac{A_{\beta}^2}{W_1 L_1}} < 1$$

$$\Rightarrow W_1 L_1 > 2.378 \times 10^{-13} \text{ m}^2$$

From eqn (3)

$$\Rightarrow 21.43 L_1^2 > 2.378 \times 10^{-13} \text{ m}^2$$

$$\Rightarrow L_1 > 105.34 \text{ nm}$$

We can take $L_1 = 200 \text{ nm}$, $W_1 = 4072 \text{ nm}$


For the switching transistors, to ensure fast switching we take minimum channel length.

$$L_2 = 50 \text{ nm}$$

$$\Rightarrow W_2 = 5026.5 \text{ nm}$$

| Parameter | M_{B1} | M_{B2} | M_1 | M_2 | V_{ES} | I_{LSB} |
|----------------|----------|----------|-------|-------|----------|------------------|
| Width (in nm) | 4070 | 4070 | 5025 | 5025 | 0.843 V | $60 \mu\text{A}$ |
| Length (in nm) | 200 | 200 | 50 | 50 | | |

Part 1 (b)

 

$$I_{REF} = R(V_{B1} - V_{B2})$$

$$V_{B1} = V_{DD} - V_{SG1}$$

$$V_{SG1} = V_{dsat1} + V_{TH}$$

$$V_{B1} = V_{DD} - V_{dsat1} - V_{TH} \quad \text{---- (1)}$$

$$V_{B2} = V_{DD} - V_{dsat1} - V_{SG2}$$

$$V_{SG2} = V_{dsat2} + V_{TH}$$

$$V_{B2} = V_{DD} - V_{dsat1} - V_{dsat2} - V_{TH} \quad \text{---- (2)}$$

Using (1) and (2),

$$V_{B1} - V_{B2} = V_{dsat2} = 0.2 \text{ V}$$

$$\Rightarrow R = \frac{0.2}{10 \times 10^{-6}} = 20 \text{ k}\Omega$$

$$I_{REF} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} V_{dsat}^2 \Rightarrow \frac{W}{L} = 3.57$$

For better matching, we can take the lengths of M_{B3} and M_{B4} to be same as M_{B1} and M_{B2}


| Parameter | MB3 | MB4 | R |
|----------------|-----|-----|--------------|
| Width (in nm) | 715 | 715 | 20k Ω |
| Length (in nm) | 200 | 200 | |

PART 2

2(a)

DC operating points obtained from DC analysis in Cadence

$$b_n = 0$$

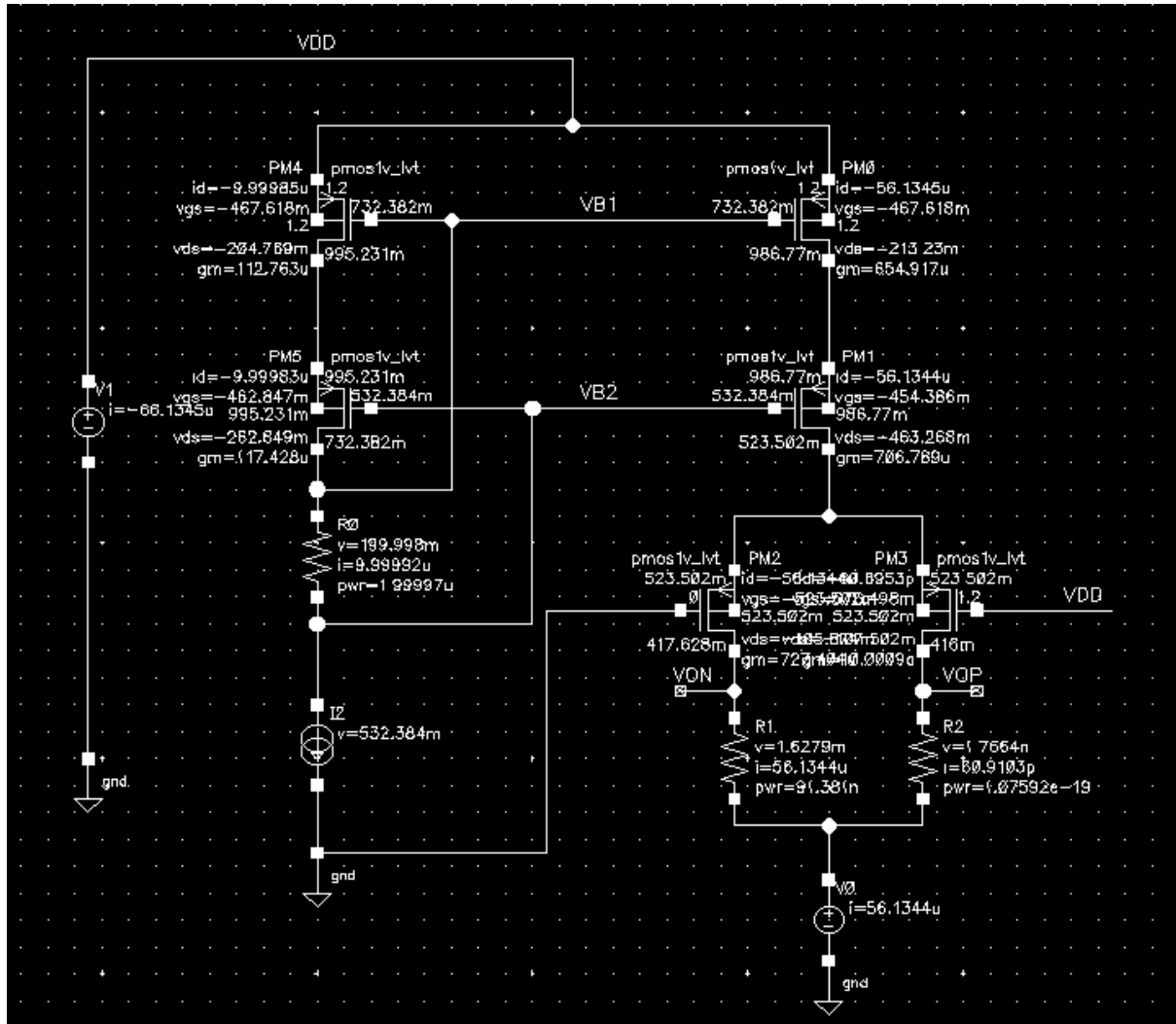

Annotated points from the figure

$$V_{B1} = 732.382 \text{ mV}$$


$$V_{B2} = 532.384 \text{ mV}$$

$$I_{LSB} = 56.135 \text{ uV}$$

$$V_{ON} = 417.628 \text{ mV}$$

$$V_{OP} = 416.000 \text{ mV}$$

$$b_n = 1$$

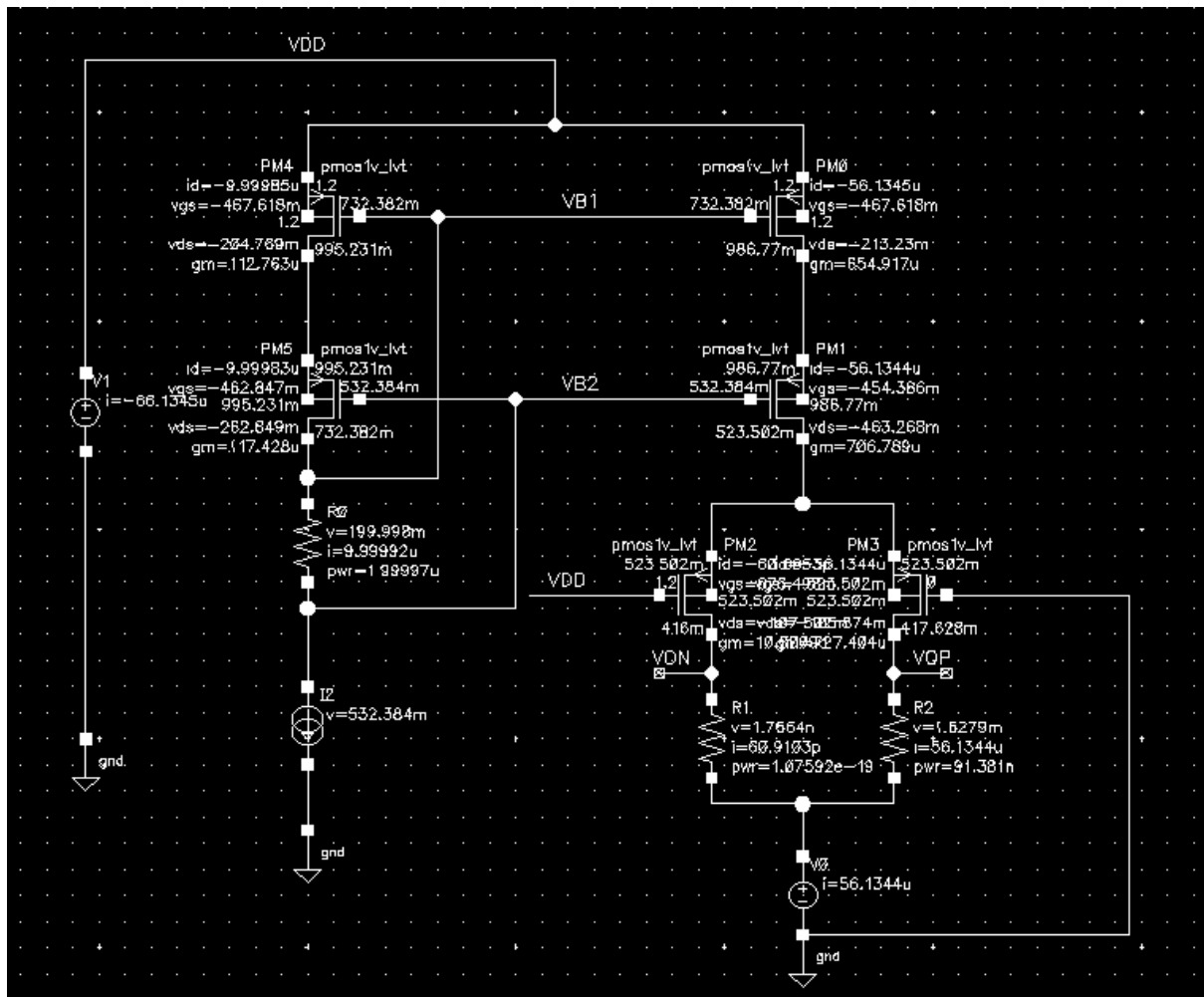

Annotated points from the figure

$$V_{B1} = 732.382 \text{ mV}$$

$$V_{B2} = 532.384 \text{ mV}$$

$$I_{LSB} = 56.135 \text{ uV}$$

$$V_{ON} = 416.000 \text{ mV}$$

$$V_{OP} = 417.628 \text{ mV}$$

Note:


V_{FS} calculated according to this measured I_{LSB} is 830 mV whereas $V_{FS} = 843 \text{ mV}$ according to the hand calculation done in part 1.

I considered 830 mV as V_{FS} when deciding my biasing voltage of $\frac{V_{FS}}{2}$.


2(b)

Inverter and Pass transistor transistor sizes adjusted to have delays within 5 ps of each other.

Inverter

 


Pass transistor

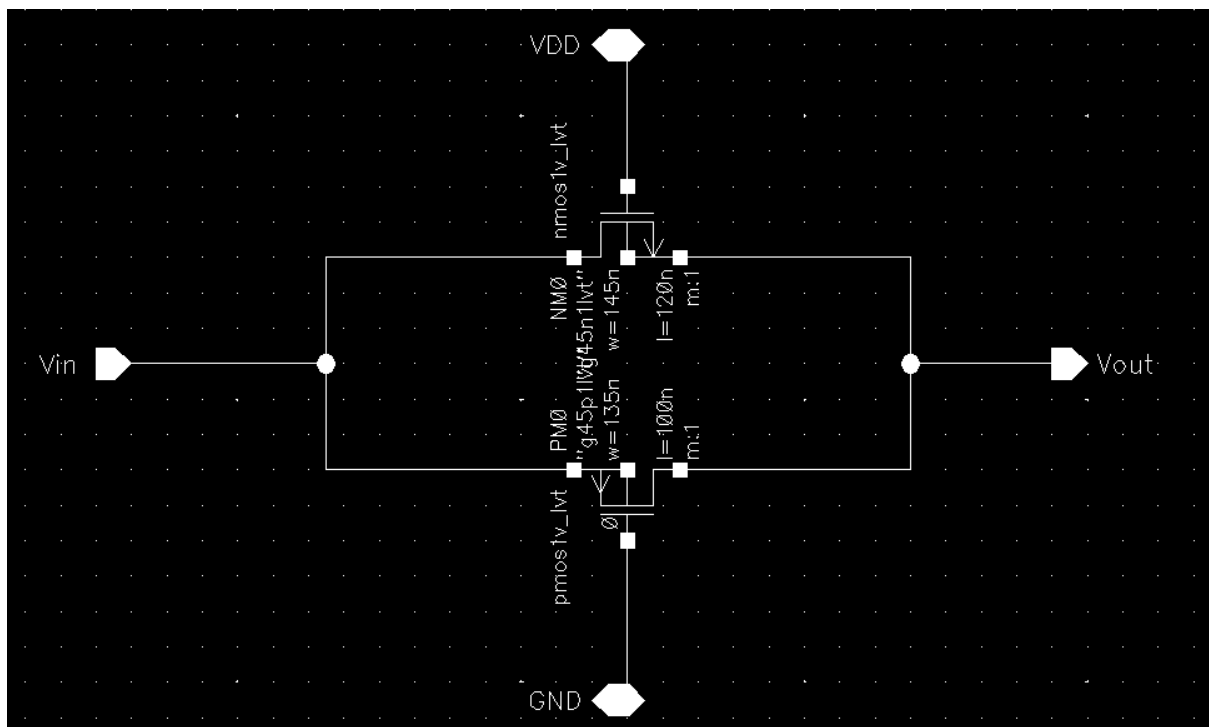

Inverter: $W_p = 305 \text{ nm}$, $L_p = 45 \text{ nm}$; $W_n = 190 \text{ nm}$, $L_n = 45 \text{ nm}$

 Pass transistor: $W_p = 135 \text{ nm}$, $L_p = 100 \text{ nm}$; $W_n = 145 \text{ nm}$, $L_n = 120 \text{ nm}$



Delay times

Inverter: 56.44 ps

Pass transistor: 51.66 ps

Difference in delays = 4.78 ps < 5 ps

Required specifications met

2(c)

Number of stages of the buffer can be calculated as

$$n = \frac{\ln\left(\frac{C_L}{C_i}\right)}{\ln(\beta)}$$

In our case,


$$\beta = 2.72$$

$$C_L = C_{gg} \text{ of } M_1 = 3.505 \text{ fF}$$

$$C_i = C_{gg} \text{ of PMOS} + \text{NMOS of the inverter} = (146.81 + 75.65) \text{ aF} = 222.46 \text{ aF}$$


$$\Rightarrow n = 2.76$$

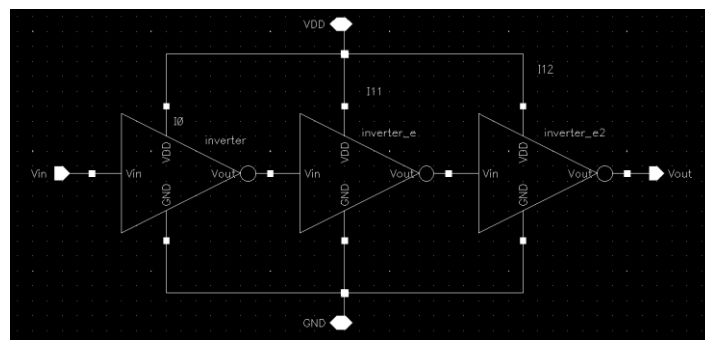Therefore, we take 3 stages in our buffer and hope it works.



| (all values in nm) | W_p | L_p | W_n | L_n |
|--------------------|-------|-------|-------|-------|
| Stage 1 | 305 | 45 | 190 | 45 |
| Stage 2 | 830 | 45 | 515 | 45 |
| Stage 3 | 2255 | 45 | 1405 | 45 |

 Transient analysis performed for 2 cycles of a 1 GHz input



In the above plot,

Rise time = Time interval between 10% and 90% of the maximum output on the rising edge


Fall time = Time interval between 90% and 10% of the maximum output on the falling edge

Accordingly,


Rise time = 13.95 ps, Fall time = 13.79 ps meet our desired specifications.

2(d)

Unit cell schematic

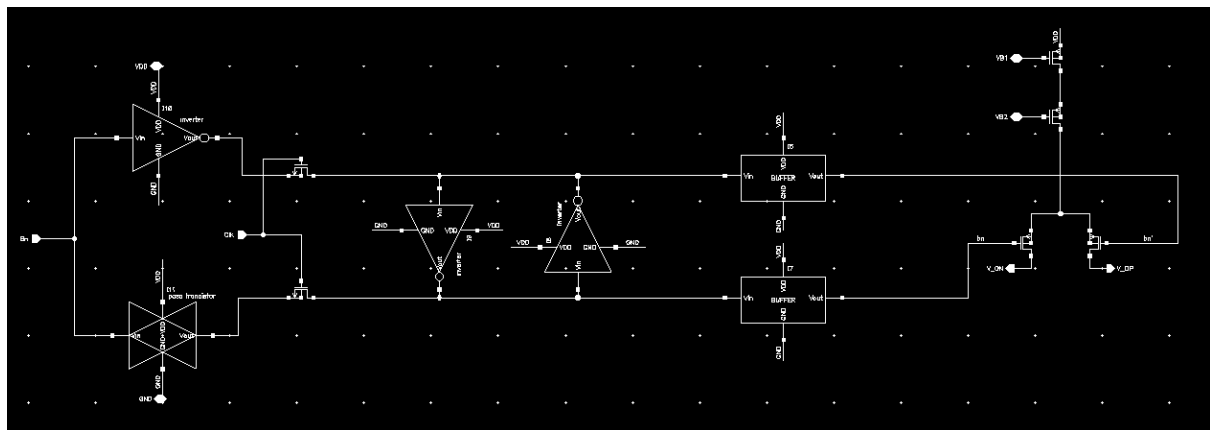

Test bench schematic

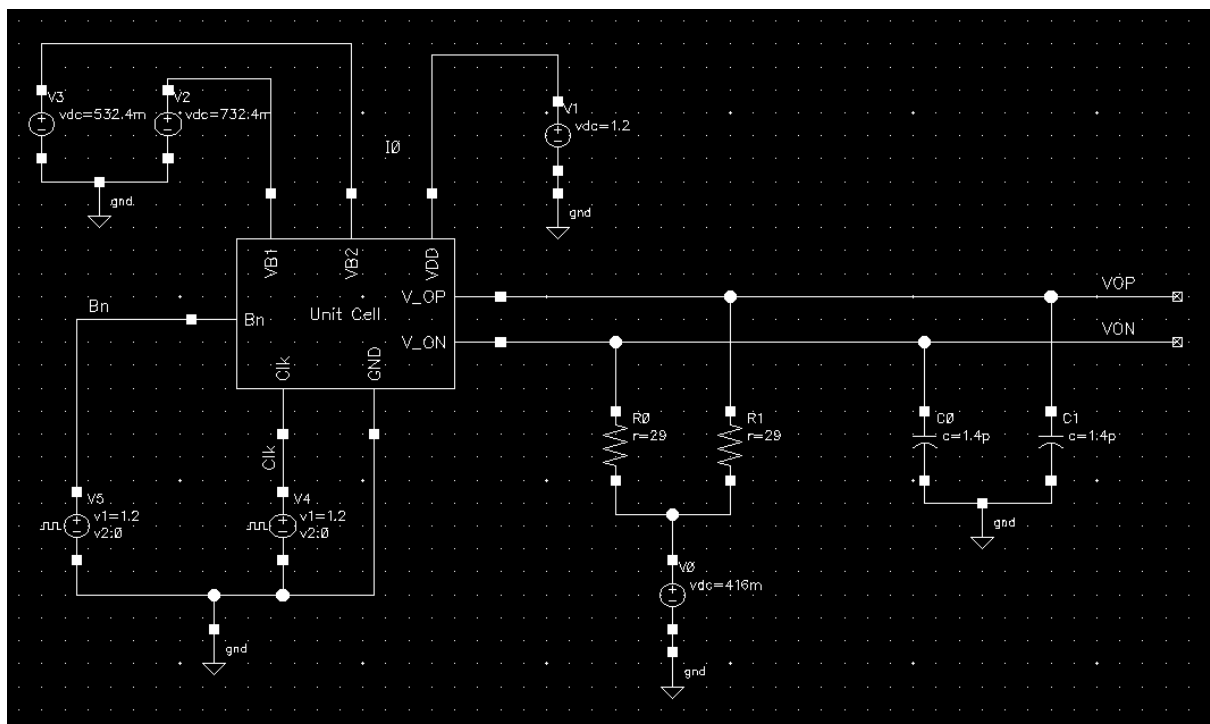


Note: $R_L = 29 \Omega$, $C_L = 1.4 pF$ taken according to the instructions given at the beginning.


Aspect ratio of the NMOS sampling switch in the unit cell: $\frac{W}{L} = \frac{500 nm}{45 nm} = 11.11$

Transient analysis performed for 4 cycles of the 1 GHz clock


Clk

 


B_n

 


b_n

 

$\overline{b_n}$

 


V_{OP}, V_{ON}

 


Region of operation

Current source transistors

MB1

 


MB2

 


(always in saturation)

Switching transistors

M1

 

M2

 

(Switching between OFF state and Saturation)

2(e)

Working of the row-column decoder

Column decoder: Takes 3 MSB's of the digital input (Let 'n' be the value of the 3 bits in decimal) and produces a thermometer output consisting 1's as the (n+1) LSB's

Row decoder: Takes the next 3 bits of the digital input and produces a thermometer output consisting 1's as the (n) least significant bits

Decoding Logic: Thermometer cells are activated according to the logic $(C_n \cdot R_n) + C_{n+1}$

According to this, in the DAC block diagram, all the thermometer cells in the first 'n' columns and the first 'n' cells in the (n+1)th column contribute to the output current I_{OP} .


Digital code ($B < 7 : 0 >$): 01010100

$$B < 7:5 > = 010$$

$$\Rightarrow \text{Column decoder output} = 00000111$$

$$B < 4:2 > = 101$$
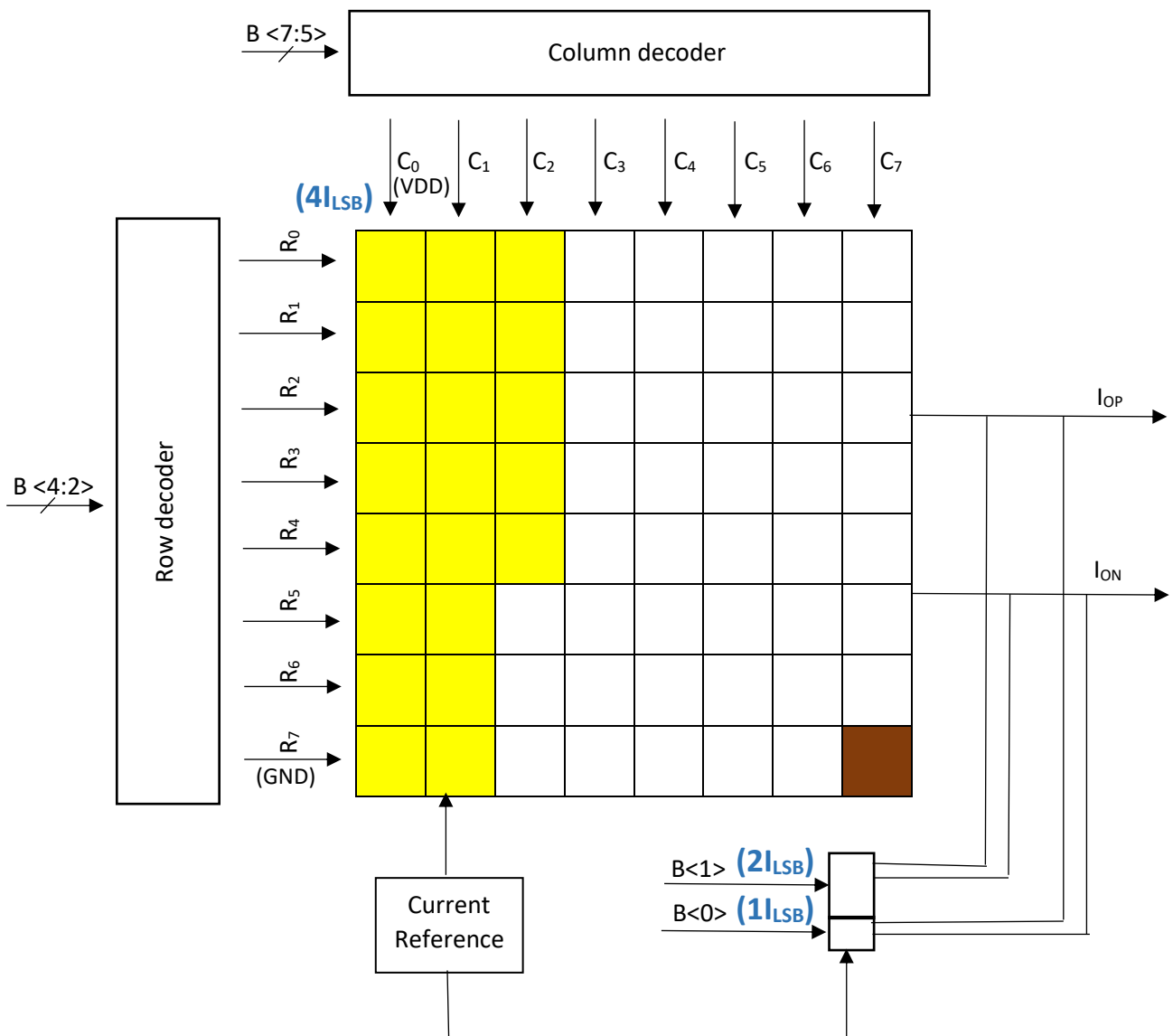
$$\Rightarrow \text{Row decoder output} = 00011111$$



Digital code ($B < 7 : 0 >$): 01110100

$$B < 7:5 > = 011$$

\Rightarrow Column decoder output = 00001111

$$B < 4:2 > = 101$$

\Rightarrow Row decoder output = 00011111

